

Assignment #5

coen210
2022 spring


Problem

Following is the simple implementation of RISC-V instruction subset (R-type, lw, sw, beq). Modify this diagram for the implementation to be able to also execute the following two instructions:

- jal
- addi

Fill the truth table for these two instructions


	I ₆	I ₅	I ₄	I ₃	I ₂	I ₁	I ₀								
	input (opcode)							ALUSrc	memtoReg	RegWrite	MemRead	MemWrite	Branch	ALUOp ₁	ALUOp ₀
R	0	1	1	0	0	1	1	0	0	1	0	0	0	1	0
lw	0	0	0	0	0	1	1	1	1	1	1	0	0	0	0
sw	0	1	0	0	0	1	1	1	x	0	0	1	0	0	0
beq	1	1	0	0	0	1	1	0	x	0	0	0	1	0	1
jal															
addi															

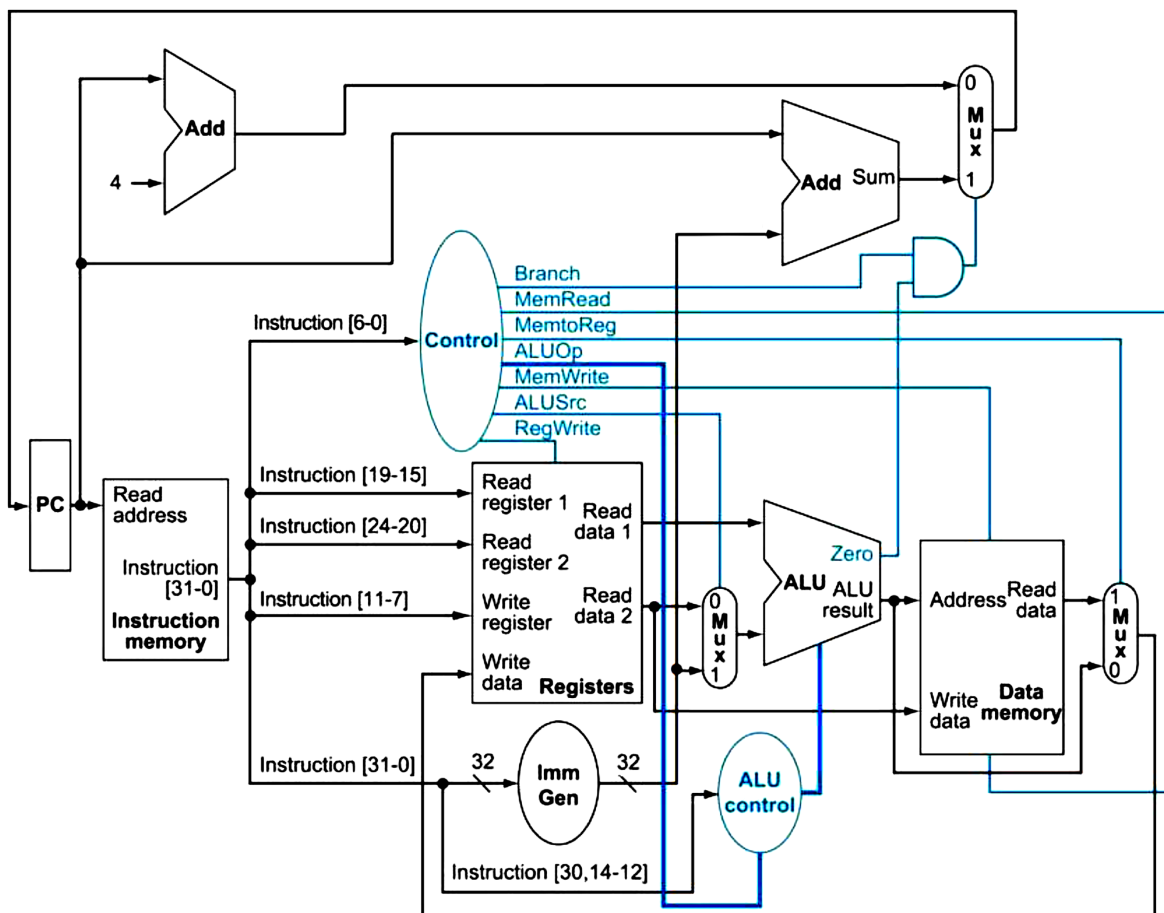

answer

Add jal to Datapath

R, lw, sw, beq
how about jal?

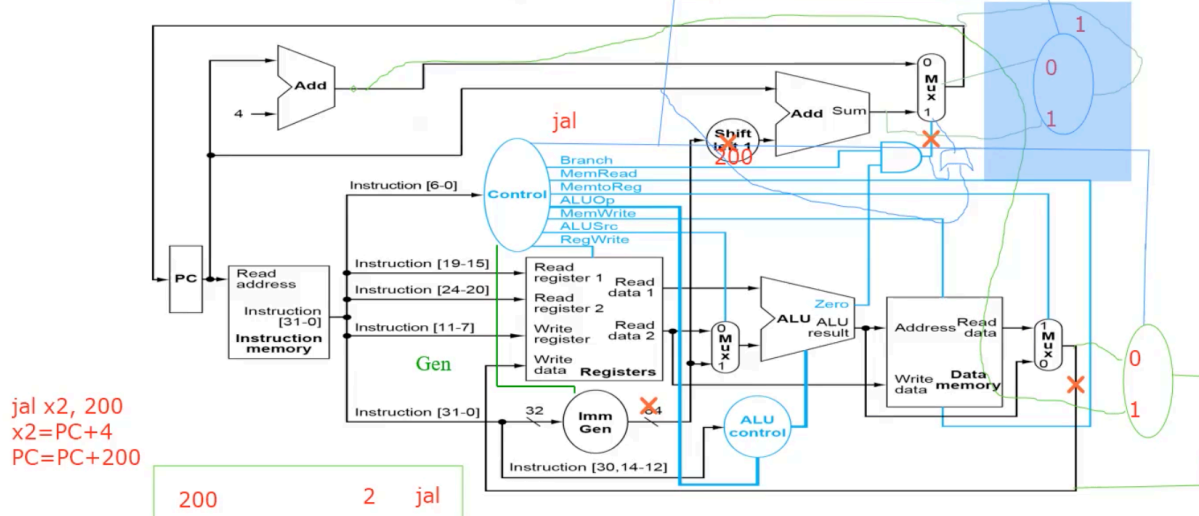

Instruction	RegWrt	Memto-Reg	Brch	Mem Read	Mem Write	ALUSrc	ALUOp1	ALUp0	Gen	jal
R-format										0
ld lw										0
sd sw										0
beq										x
jal	1	x	x	0	0	x	x	x	UJ	1

27



(note: the order of this table is different from the above table.)

BEQ Instruction

```
addi x2, x4, 8 //x2=x4+8
```

